

## Experiment 1: Low Pass Filter and Inverting Amplifier

### Aims of the experiment

You will get acquainted to the lab instruments (digital oscilloscope, wave generator, multimeters, power supplies) and you will work with fundamental electronic circuits.

### Theoretical Background

#### RC Low Pass Filter

An RC low pass filter as shown in fig. 1.1 attenuates signals of frequencies higher than the cut off frequency  $f_{co}$ . The cut off frequency depends on the capacitance C and the resistance R.

$$f_{co} = \frac{1}{2\pi RC}$$

At the cut off frequency the output signal  $U_{out}$  has dropped to a value of  $\frac{1}{\sqrt{2}}$  of the original value at low frequencies.

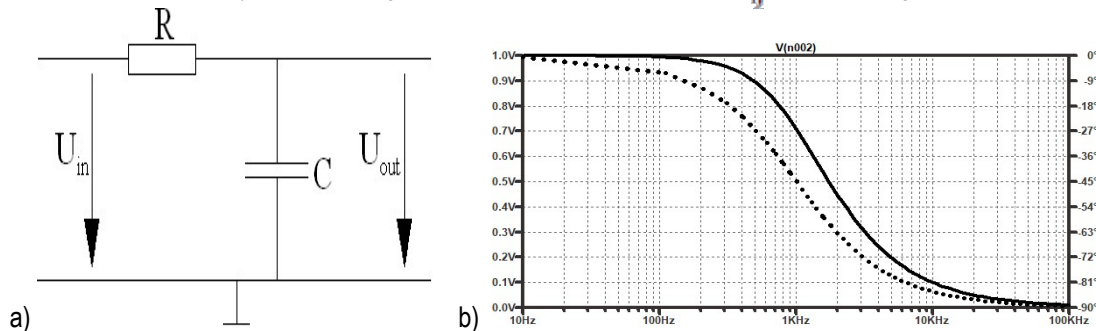


Fig. 1.1 a) RC low pass filter b) Amplitude ratio A and phase  $\varphi$  as function of the frequency f.

#### Charging and Discharging of a Capacitor

The differential equation for the RC low pass as shown in fig. 1.1 is given by

$$U_{in} = \tau \cdot \frac{dU_{out}}{dt} + U_{out}$$

where  $\tau = RC$  is the time constant,  $U_{in}$  the input voltage and  $U_{out}$  the output voltage.

For  $U_{in} = 0$  the solution of the differential equation is (**discharging of a capacitor**)

$$U_{out}(t) = U_0 \cdot e^{-\frac{t}{\tau}} \quad \text{for } t = \tau: U_{out} = 36,8\% \cdot U_0$$

where  $U_0$  is the voltage of the capacitor at the start ( $U_0$  is the supply voltage for a fully charged capacitor).

For  $U_{in} = U_0$  the solution is (**charging of a capacitor**)

$$U_{out}(t) = U_0 \left( 1 - e^{-\frac{t}{\tau}} \right) \quad \text{for } t = \tau: U_{out} = 63,2\% \cdot U_0$$

These solutions can be used to determine the time constant  $\tau$  in exercise 2.

#### Inverting Operational Amplifier

Fig. 1.2 shows an inverting operational amplifier. The output voltage  $U_{out}$  as a function of the input voltage  $U_{in}$  is given by

$$U_{out} = -\frac{R_2}{R_1} U_{in}$$

If the frequency of  $U_{in}$  goes above the cut off frequency of the amplifier circuit,  $U_{out}$  drops below the value calculated by the above equation. At the cut off frequency the output has dropped to a value of  $\frac{1}{\sqrt{2}}$  of the original value.

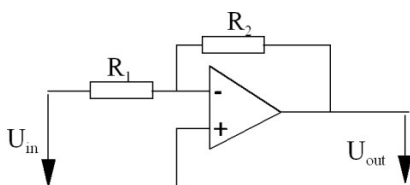


Fig 1.2 Inverting operational amplifier.

**Exercise 1: Frequency Response of an RC Low Pass Filter**

Build up the RC-low-pass filter as shown in fig. 1.3 with  $R = 10\text{ k}\Omega$ ,  $C = 100\text{ nF}$ . Connect the wave generator to the circuit and connect channel 1 of the digital storage oscilloscope (DSO) to the input and channel 2 of the DSO to the output of the low pass circuit.

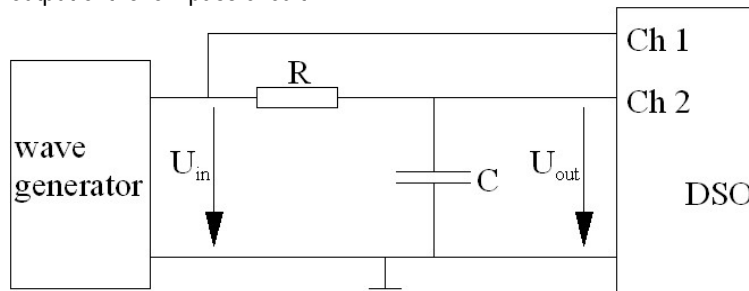


Fig. 1.3: RC low pass filter connected to the wave generator and the digital storage oscilloscope DSO.

Provide a **sine wave** of varying frequency  $f$  as input starting with a low frequency (e. g.  $f = 1\text{ Hz}$ ,  $U_{in} = 10\text{ Vpp}$ ). For each frequency value measure the input amplitude  $U_{in}$  and the output amplitude  $U_{out}$  and calculate the **ratio  $A = U_{out}/U_{in}$** . Determine the **phase shift  $\phi$**  between the output and the input signal both by counting divisions on the DSO-screen and by using the direct measurement tool of the DSO (not available for all DSOs in the lab). Consider that a full period of the sine wave relates to  $360^\circ$ . Increase the frequency to a value that you obtain a ratio  $A$  of 0.9, 0.8, ... 0.1 and fill the table of the lab protocol with your measurement values.

In the lab report, draw a diagram of the ratio  $A$  and the phase  $\phi$  as a function of the frequency  $f$  based on your measurement values. Determine the **cut off frequency  $f_{co}$**  and compare it to the **calculated value** according to the above equation. What is the value of the phase at the cut off frequency?

**Exercise 2: Step Response of the RC Low Pass Filter**

a) Instead of the sine signal apply a **positive square wave** with the amplitude  $U_0 = 10\text{ V}$  to the low pass circuit.

Choose a frequency significantly **below the cut off frequency**. Measure the input signal  $U_{in}$  and the output signal  $U_{out}$  and **record the signals**. Determine the **time constant  $\tau$**  on the rising and on the falling edge of the signal and compare it to the calculated time constant  $\tau$ . Include the recorded signals into your lab report.

b) Now apply a positive square wave with a frequency significantly **above the cut off frequency**. Again measure the input signal  $U_{in}$  and the output signal  $U_{out}$  and record the signals (to be included in the lab report). Explain the curve.

**Exercise 3: Frequency Response of an Inverting Operational Amplifier**

a) Implement an **inverting OP-amplifier** as depicted in fig 1.2 with  $R_1 = 1\text{ k}\Omega$  and  $R_2 = 1\text{ k}\Omega$ . Supply a sine wave as input voltage  $U_{in}$  (e. g.  $U_{in} = 2\text{ Vpp}$ ) and measure both the input voltage  $U_{in}$  and the output voltage  $U_{out}$  with the DSO. Similar to exercise 1, determine the **ratio  $A$**  between output and input amplitude **as a function of the frequency**.

Determine the **cut off frequency  $f_{co}$** .

b) Exchange resistor  $R_2$  with  $10\text{ k}\Omega$  (suggested  $U_{in} = 1\text{ Vpp}$ ), again determine the ratio  $A$  as a function of the frequency and determine the cut off frequency  $f_{co}$ .

**Acknowledgement**

We thank Prof. Dr. B. Deppisch for providing the previous lab instruction material.

Names		Date of Experiment

## Lab Protocol: Experiment 1: Low Pass Filter and Inverting Amplifier

### Exercise 1: Frequency Response of an RC Low Pass

#### To be done before the lab

Calculate the cut off frequency  $f_{co}$   
for the given low pass filter.

freq. f	$U_{in}$ [V]	$U_{out}$ [V]	A	$\phi$ [°]
			1	
			0.9	
			0.8	
			0.7	
			0.6	
			0.5	
			0.4	
			0.2	

Determined cut off frequency $f_{co}$	
Phase angle $\phi$ at cut off frequency	

**Exercise 2: Step Response of the RC Low Pass Filter****To be done before the lab**

Calculate the time constant  $\tau$   
from the values of the components  
as given in the instruction text.

chosen frequency	
Measured time constant $\tau$ on rising edge	
on falling edge	

**Exercise 3: Frequency Response of an Inverting Operational Amplifier**

a)  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ .

frequency $f$	$U_{in} [\text{V}]$	$U_{out} [\text{V}]$	A
			1
			0.9
			0.8
			0.7
			0.6
			0.4
			0.2

Determined cut off frequency $f_{co}$	
---------------------------------------	--

b)  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ .

frequency $f$	$U_{in} [\text{V}]$	$U_{out} [\text{V}]$	A
			10
			9
			8
			7
			6
			4
			2

Determined cut off frequency $f_{co}$	
---------------------------------------	--

Lab protocol approved